


Electronic Circuit Design and Experiment II Project

2024






Project Goals

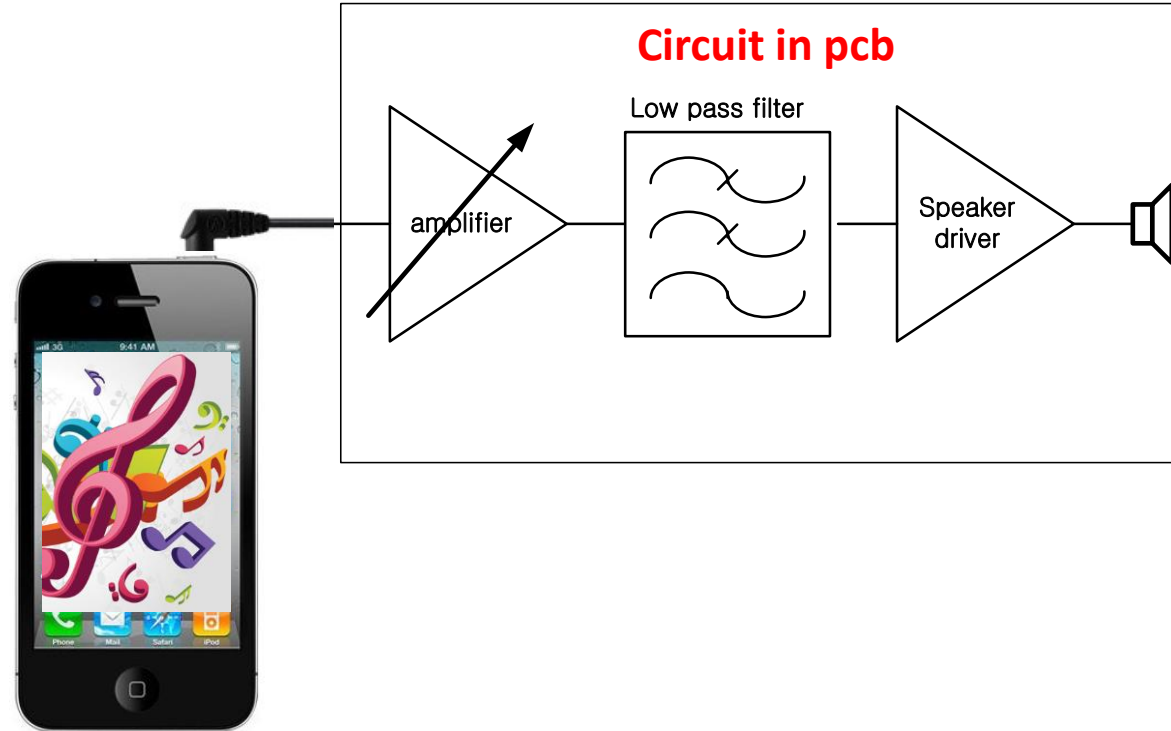Implementation of a Speaker Driver Circuit with a Low Pass Filter



Project Description

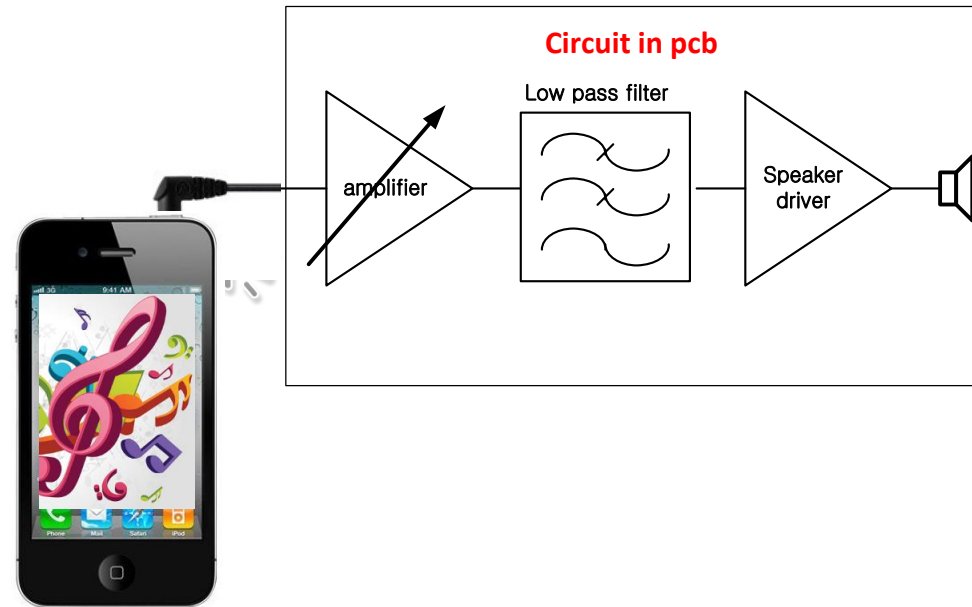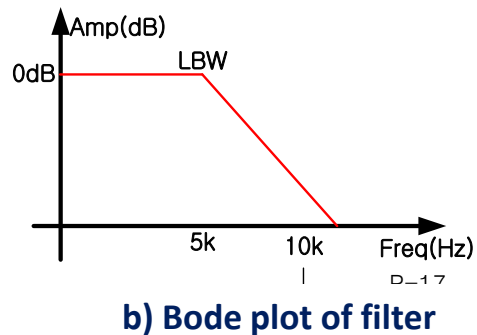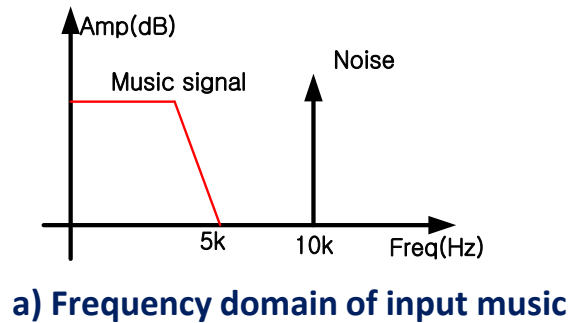1. The audio source (MP3) currently has noise (single tone) at 10kHz. See the figure (a) below.




2. The speaker driving system we are designing needs to include a filter to remove 10kHz noise.
3. Although humans can hear frequencies from 20Hz to 20,000Hz, typically only frequencies below 5kHz are perceived as important signals in most music.
4. Therefore, the system should include a low-pass filter that minimizes noise at 10kHz while preserving frequencies below 5kHz with minimal distortion.
5. The amplifier should have adjustable gain, which can be achieved using a variable resistor.
6. The speaker driver will use the LM741 (UA741) operational amplifier.

最小畸变

Project Schedule

	Tue	비고	contents
11w	11/12		Project Orientation / PSPICE simulation (submit report)
12w	11/19		PADS Schematic
13w	supplementary course		PADS Schematic& Layout
14w	11/26		PADS Layout (submit CAM file)
15w	12/10		PCB soldering
16w	12/17		PCB soldering & test


Circuit Configuration

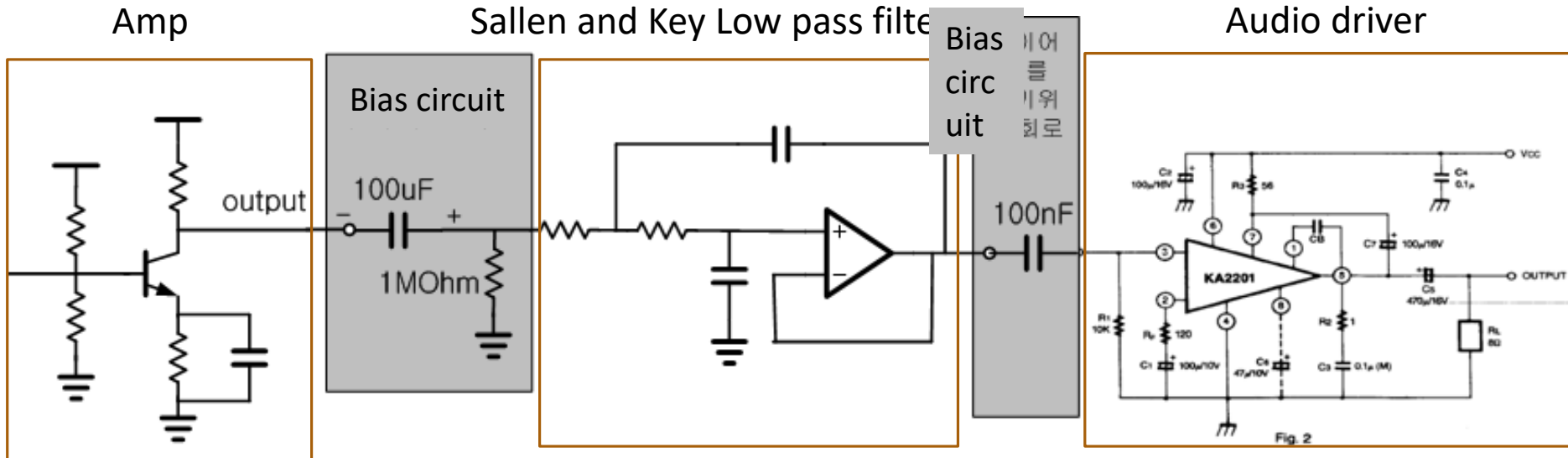

1. Configure an amplifier and a low-pass filter for simulation
2. Design a low-pass filter that minimizes noise at 10 kHz while minimally distorting frequencies below 5 kHz
3. The amplifier's gain should be adjustable


1. PSpICE Simulation

Amp & Low pass filter

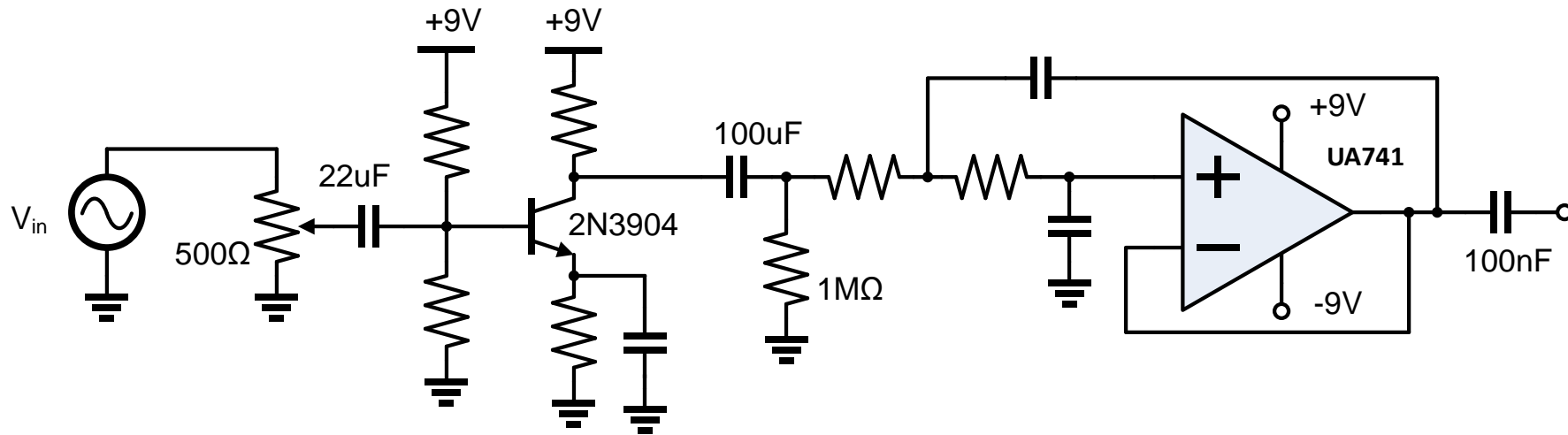


1. PSPICE Simulation

Example)

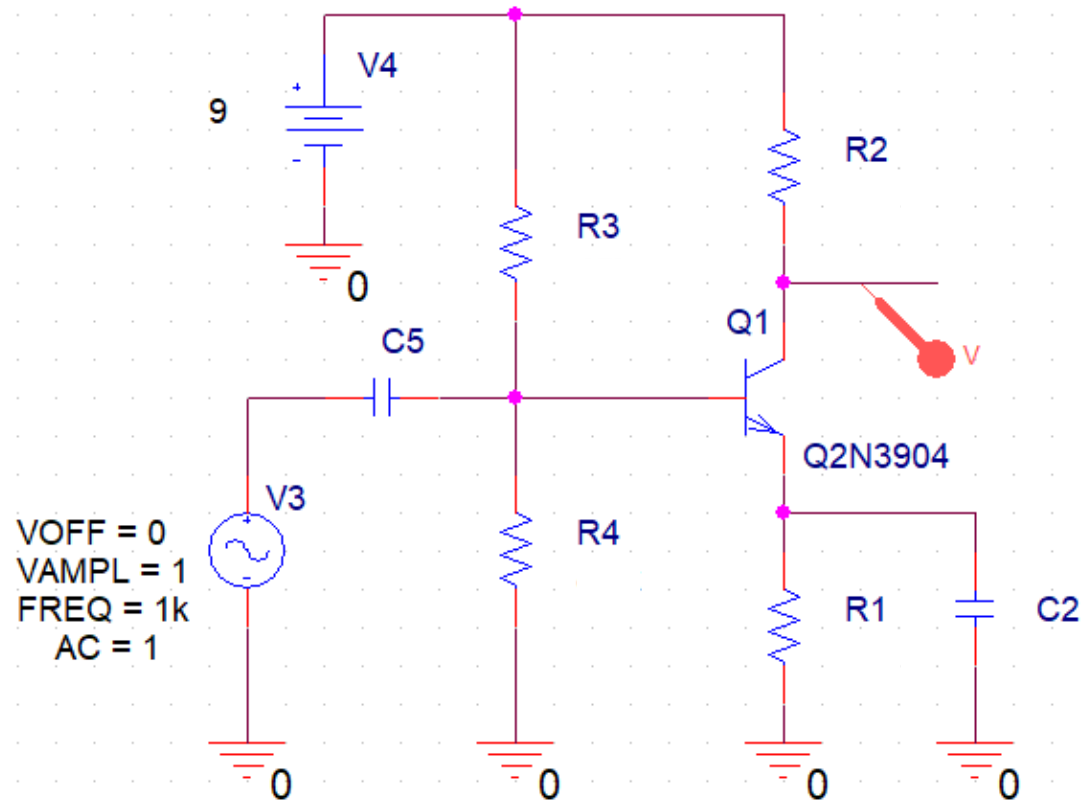


1. PSpICE Simulation

Example)

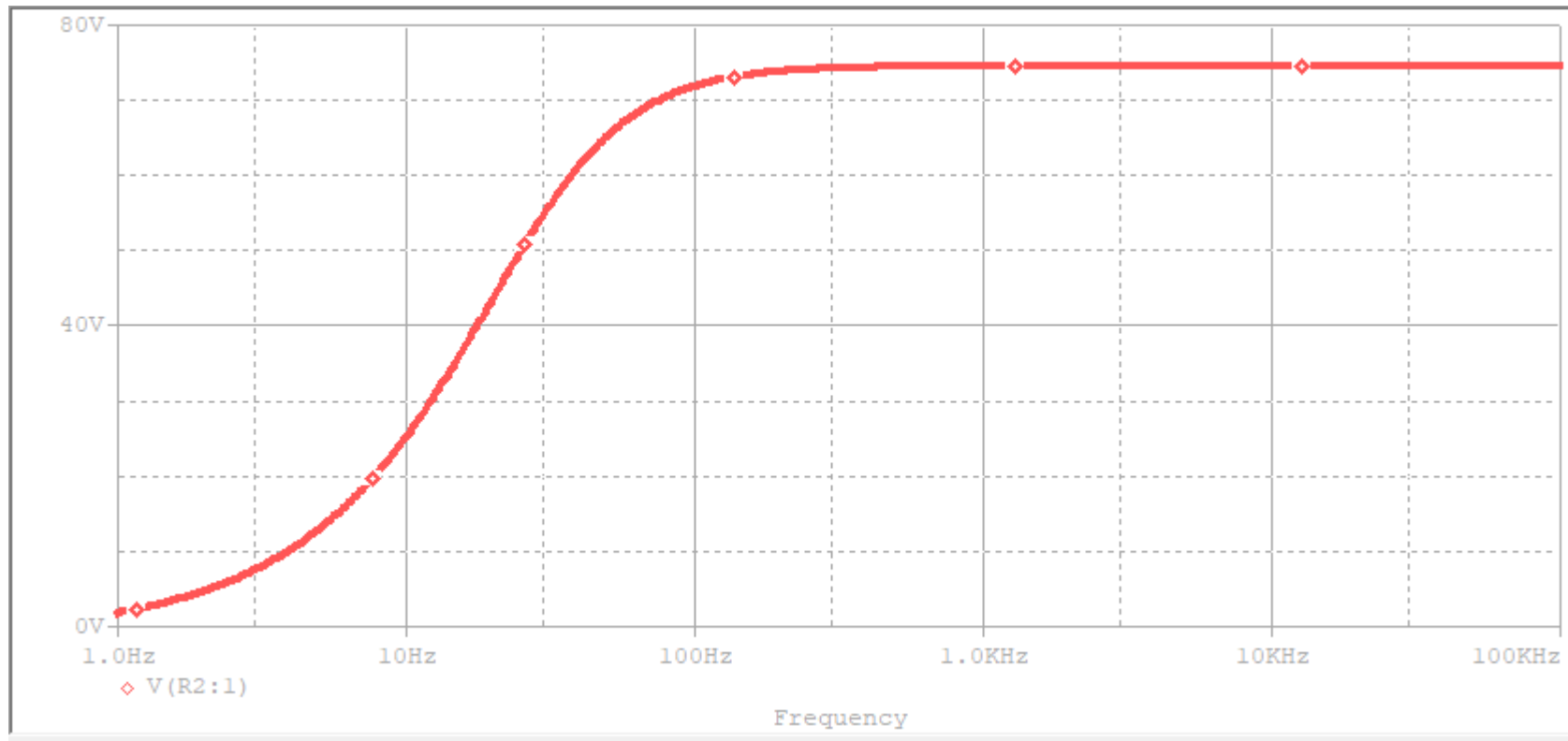


1. PSpICE Simulation

Example)

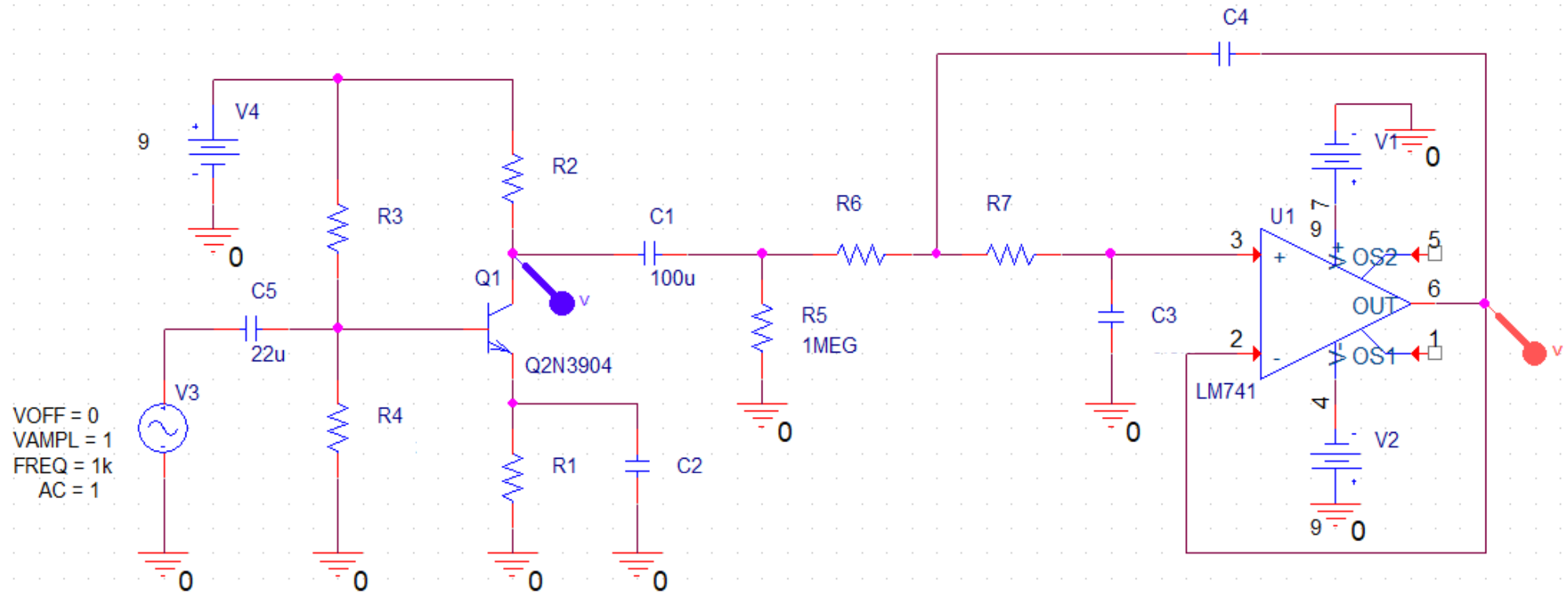

1. PSpICE Simulation

Example)

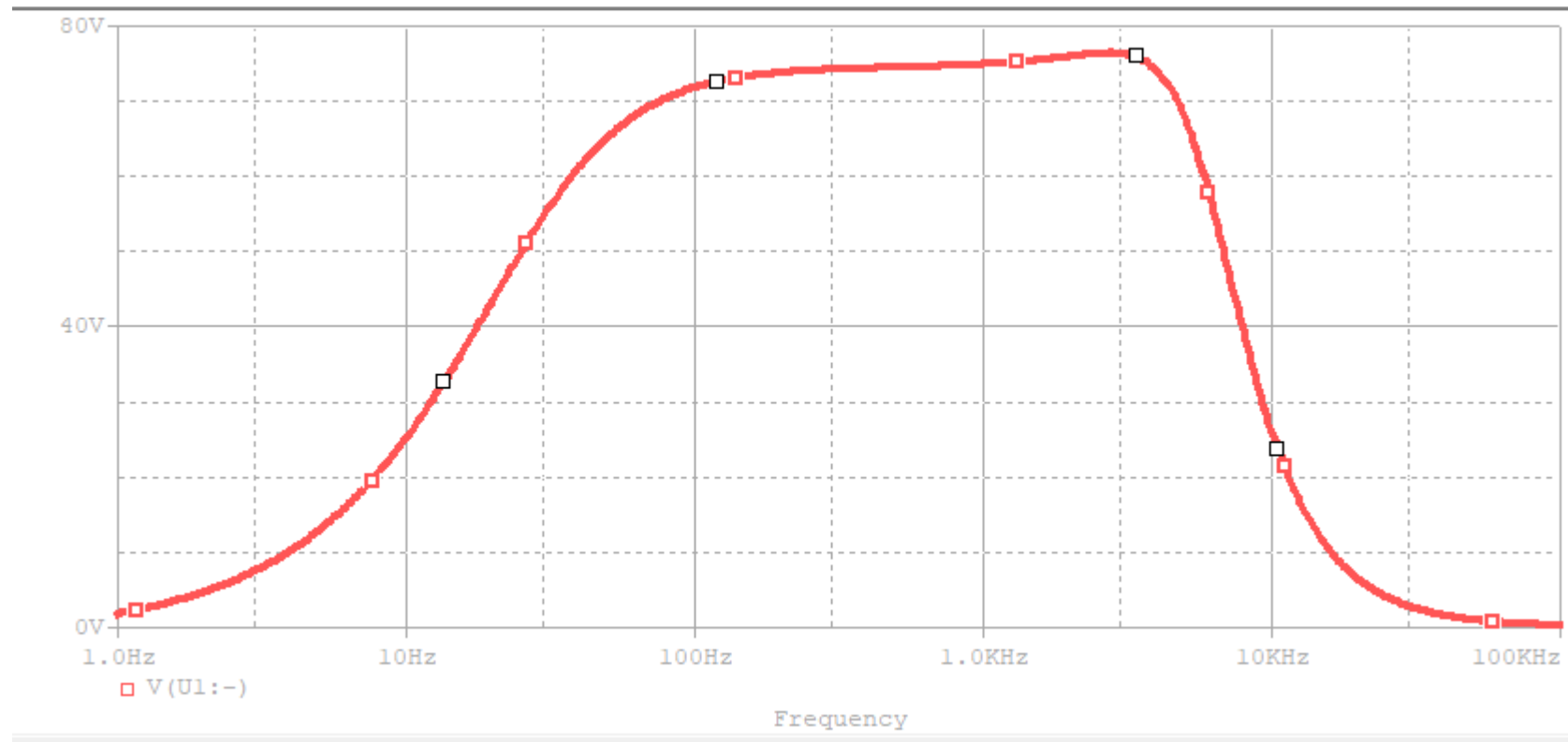

1. PSPICE Simulation

00AW'S ELECTRONICS LABORATORY <small>http://blog.gowat.com/author/4067</small>							
1.0pF	10pF	100pF	1.0nF	10nF	100nF	1.0uF	10uF
1.2pF	12pF	120pF	1.2nF	12nF	120nF	1.2uF	12uF
1.5pF	15pF	150pF	1.5nF	15nF	150nF	1.5uF	15uF
1.8pF	18pF	180pF	1.8nF	18nF	180nF	1.8uF	18uF
2.2pF	22pF	220pF	2.2nF	22nF	220nF	2.2uF	22uF
2.7pF	27pF	270pF	2.7nF	27nF	270nF	2.7uF	27uF
3.3pF	33pF	330pF	3.3nF	33nF	330nF	3.3uF	33uF
3.9pF	39pF	390pF	3.9nF	39nF	390nF	3.9uF	39uF
4.7pF	47pF	470pF	4.7nF	47nF	470nF	4.7uF	47uF
5.6pF	56pF	560pF	5.6nF	56nF	560nF	5.6uF	56uF
6.8pF	68pF	680pF	6.8nF	68nF	680nF	6.8uF	68uF

100nF	1.0uF	10uF	100uF	1.0F	10F	100F	378uF	4.6F	50F
150nF	1.5uF	12uF	108uF	1.1F	11F	110F	380uF	4.7F	55F
220nF	2.0uF	15uF	120uF	1.2F	12F	120F	390uF	4.8F	56F
330nF	2.2uF	16uF	124uF	1.3F	13F	150F	400uF	5.0F	60F
470nF	3.0uF	18uF	130uF	1.4F	15F	220F	420uF	5.1F	62F
680nF	3.3uF	20uF	140uF	1.5F	16F	330F	430uF	5.4F	66F
	4.0uF	21uF	145uF	1.6F	17F	470F	450uF	5.5F	68F
	4.7uF	22uF	150uF	1.7F	18F	666F	460uF	5.6F	76F
	5.0uF	24uF	161uF	1.8F	20F		470uF	5.8F	
	5.6uF	25uF	170uF	2.0F	22F		480uF	6.0F	
	6.8uF	27uF	180uF	2.1F	23F		500uF	6.5F	
	7.0uF	30uF	189uF	2.2F	24F		510uF	6.8F	
	8.0uF	33uF	200uF	2.5F	25F		520uF	7.2F	
	8.2uF	35uF	210uF	2.6F	26F		540uF	7.4F	
		36uF	216uF	2.7F	27F		550uF	7.6F	
		39uF	220uF	2.8F	28F		560uF	7.8F	
		40uF	230uF	2.9F	30F		590uF	8.2F	
		43uF	233uF	3.0F	31F		620uF	8.3F	
		47uF	240uF	3.1F	32F		645uF	8.4F	
		50uF	243uF	3.3F	33F		650uF	8.7F	
		53uF	250uF	3.4F	34F		680uF	9.0F	
		56uF	270uF	3.5F	36F		700uF	9.6F	
		60uF	300uF	3.6F	37F		708uF		
		68uF	320uF	3.7F	38F		730uF		
		72uF	324uF	3.9F	39F		800uF		
		75uF	330uF	4.0F	40F		820uF		
		82uF	340uF	4.1F	41F		850uF		
		88uF	350uF	4.2F	47F		860uF		
			370uF	4.3F	48F				

00AW'S
ELECTRONICS
LABORATORY
http://blog.gowat.com/author/4067

1. PSPICE Simulation

1.0	10	100	1.0K	10K	100K	1.0M
1.1	11	110	1.1K	11K	110K	1.1M
1.2	12	120	1.2K	12K	120K	1.2M
1.3	13	130	1.3K	13K	130K	1.3M
1.5	15	150	1.5K	15K	150K	1.5M
1.6	16	160	1.6K	16K	160K	1.6M
1.8	18	180	1.8K	18K	180K	1.8M
2.0	20	200	2.0K	20K	200K	2.0M
2.2	22	220	2.2K	22K	220K	2.2M
2.4	24	240	2.4K	24K	240K	2.4M
2.7	27	270	2.7K	27K	270K	2.7M
3.0	30	300	3.0K	30K	300K	3.0M
3.3	33	330	3.3K	33K	330K	3.3M
3.6	36	360	3.6K	36K	360K	3.6M
3.9	39	390	3.9K	39K	390K	3.9M
4.3	43	430	4.3K	43K	430K	4.3M
4.7	47	470	4.7K	47K	470K	4.7M
5.1	51	510	5.1K	51K	510K	5.1M
5.6	56	560	5.6K	56K	560K	5.6M
6.2	62	620	6.2K	62K	620K	6.2M
6.8	68	680	6.8K	68K	680K	6.8M
7.5	75	750	7.5K	75K	750K	7.5M
8.2	82	820	8.2K	82K	820K	8.2M
9.1	91	910	9.1K	91K	910K	9.1M

1. PSPICE Simulation

Audio driver

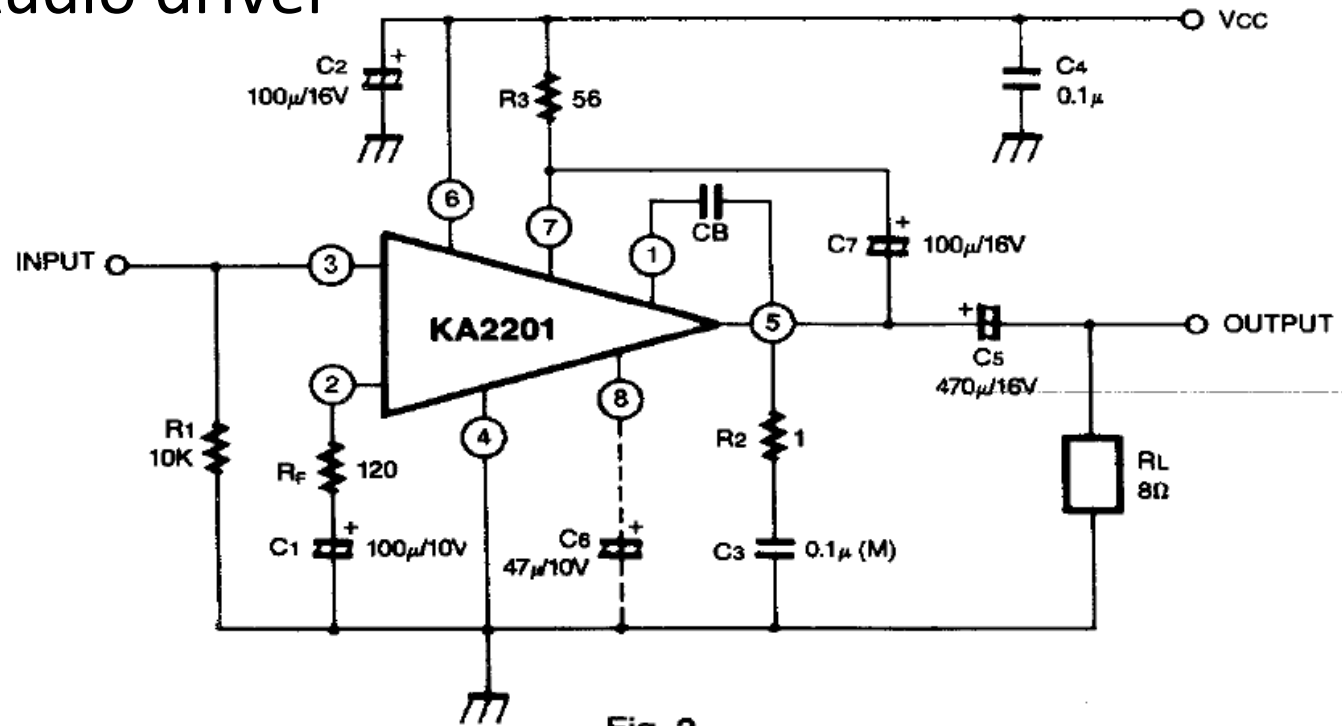


Fig. 2


The audio driver is excluded from the PSPICE simulation due to the absence of a SPICE model

2. PCB



1. Using the PADS Tool distributed by the teaching assistant, create the CAM file and proceed with ordering

3. Speaker measurement

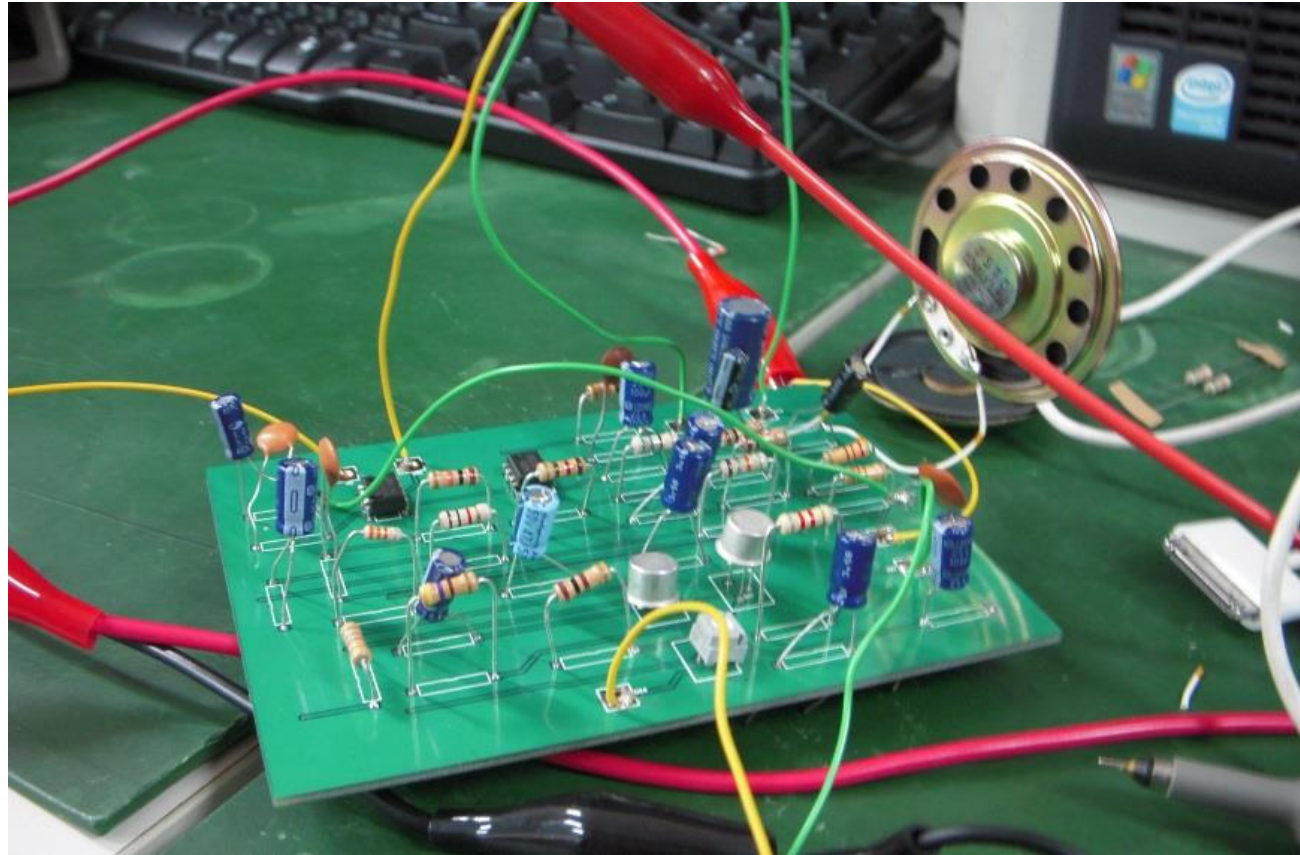

4. Result report

PSPICE simulation & background theory

Summary

- We will design a speaker.
- The speaker consists of an amplifier, low-pass filter, and audio driver.
- You should design the amplifier and low-pass filter.
- You can simulate the amplifier and low-pass filter performance in PSpice.
- By 11:59 p.m. next Monday, you must design an amplifier and low-pass filter that meet the specified conditions and **submit a design report.**
- Starting next Tuesday, we will use a tool called PADS to create a PCB for implementing the speaker you designed.